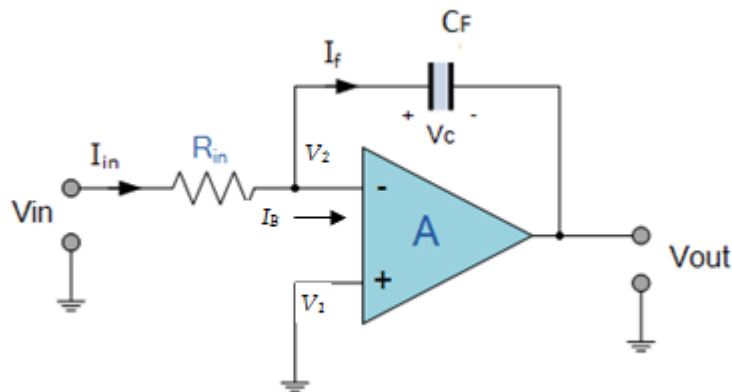


THE OPERATIONAL AMPLIFIER

THE INTEGRATOR

A circuit in which the output voltage waveform is the integral of the input waveform is the *integrator* or the *integration amplifier*. Such a circuit is obtained by using a basic inverting amplifier configuration if the feedback resistor R_F is replaced by a capacitor C_F .



The expression for the output voltage V_o can be obtained by writing Kirchhoff's current equation at node V_2

$$I_{in} = I_B + I_f$$

Since I_B is negligibly small,

$$I_{in} \cong I_f$$

The relationship between current through and voltage across the capacitor is

$$i_c = C \frac{dV_c}{dt}$$

Therefore

$$\frac{V_{in} - V_2}{R_{in}} = C_F \frac{d}{dt} (V_2 - V_{out})$$

However $V_1 = V_2 \cong 0$ because A (input impedance of OPAMP) is very large therefore

$$\frac{V_{in}}{R_{in}} = C_F \frac{d}{dt} (-V_{out})$$

The output voltage can be obtained by integrating both sides with respect to time


$$\begin{aligned} \int_0^t \frac{V_{in}}{R_{in}} dt &= \int_0^t C_F \frac{d}{dt} (-V_{out}) dt \\ &= C_F (-V_{out}) \end{aligned}$$

Therefore

$$V_{out} = -\frac{1}{R_{in} C_F} \int_0^t \frac{V_{in}}{R_{in}} dt + C \quad [1]$$

Where C is the integration constant and is proportional to the value of the output voltage V_{out} at time $t=0$ seconds.

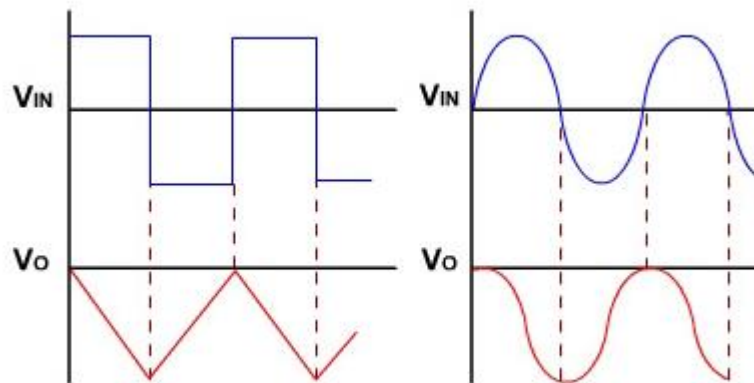
Equation [1] indicates that the output voltage is directly proportional to negative integral of input voltage and inversely proportional to time constant ($R_{in} C_F$). For example, if the input is sine wave, the output is cosine wave; or if the input is square wave, the output will be triangular wave.



Operational Amplifier Integrator Waveforms

THE DIFFERENTIATOR

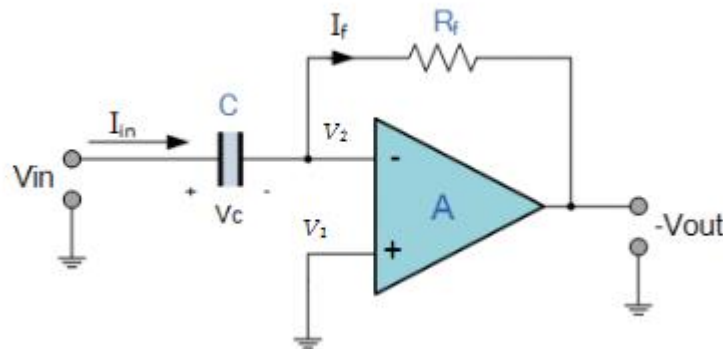A circuit in which the output voltage waveform is the derivative of the input waveform is the *differentiator* or the *differentiation amplifier*. Such a circuit is obtained by using a basic inverting amplifier configuration if the input resistor R_{in} is replaced by a capacitor C .



The expression for the output voltage V_{out} can be obtained by writing Kirchhoff's current equation at node V_2

$$I_{in} = I_B + I_f$$

Since I_B is negligibly small,

$$I_{in} \cong I_f$$


$$C \frac{d}{dt} (V_{in} - V_2) = \frac{V_2 - V_{out}}{R_f}$$

However $V_1 = V_2 \cong 0$ because A (input impedance of OPAMP) is very large therefore

$$C \frac{d}{dt} (V_{in}) = \frac{-V_{out}}{R_f}$$

$$V_{out} = -CR_f \frac{d}{dt} (V_{in}) \quad [1]$$

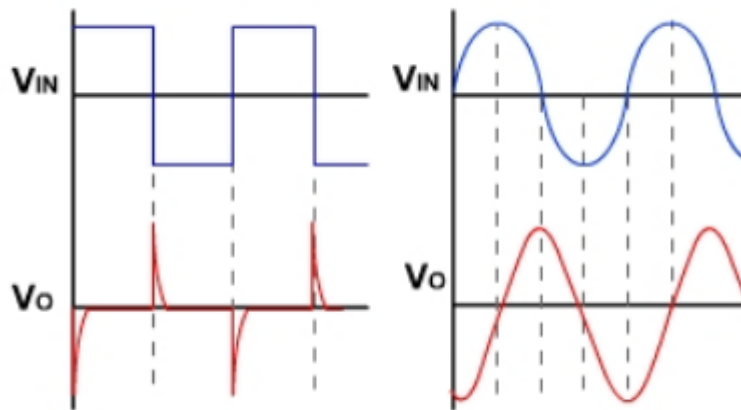Thus the output voltage V_{out} is equal to CR_f times negative instantaneous rate of change of input voltage V_{in} with time. The cosine wave produce sine output or square input will produce a spike wave output.



Operational Amplifier Differentiator Waveforms

COMPARATOR

A Comparator is a circuit which compares a signal voltage at one input of an OPAMP known as reference at the other input.

When the non-inverting voltage is greater than the inverting voltage, the comparator produces high output voltage equal to the positive saturation voltage.

When the non-inverting voltage is less than the inverting voltage, the comparator produces low output voltage equal to the negative saturation voltage.

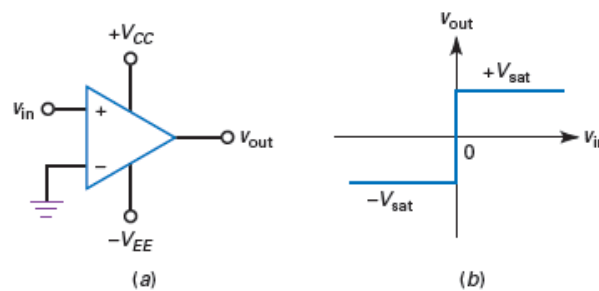


Fig. 1 (a) Comparator; (b) input/output response.

The simplest way to build a comparator is to connect an op amp without feedback resistors, as shown in Fig. 1(a). Because of the high open-loop voltage gain, a positive input voltage produces positive saturation, and a negative input voltage produces negative saturation. The comparator of Fig. 1(a) is called a **zero-crossing detector** because the output voltage ideally switches from low to high or vice versa whenever the input voltage crosses zero. Figure 1(b) shows the input-output response of a zero-crossing detector.

Comparators with Nonzero References

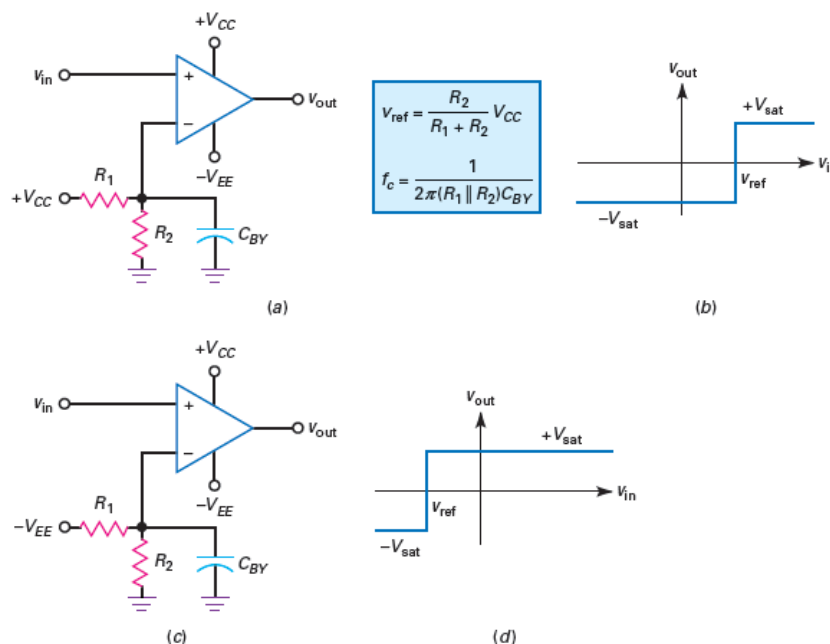


Figure 2 (a) Positive threshold; (b) positive input/output response; (c) negative threshold; (d) negative input/output response

The voltage divider produces the following reference voltage for the inverting input

$$V_{ref} = \frac{R_2}{R_1 + R_2} V_{CC}$$

When V_{in} is greater than V_{ref} , the differential input voltage is positive and the output voltage is high. When V_{in} is less than V_{ref} , the differential input voltage is negative and the output voltage is low. Figure 2 (b) shows the **transfer characteristic** (input/output response). The trip point is now equal to V_{ref} . When V_{in} is greater than V_{ref} , the output of the comparator goes into positive saturation. When V_{in} is less than V_{ref} , the output goes into negative saturation.

If a negative limit is preferred, connect $-V_{EE}$ to the voltage divider, as shown in Fig. 2 (c). Now a negative reference voltage is applied to the inverting input. When V_{in} is more positive than V_{ref} , the differential input voltage is positive and the output is high, as shown in Fig. 2(d). When V_{in} is more negative than V_{ref} , the output is low.

SCHMITT TRIGGER

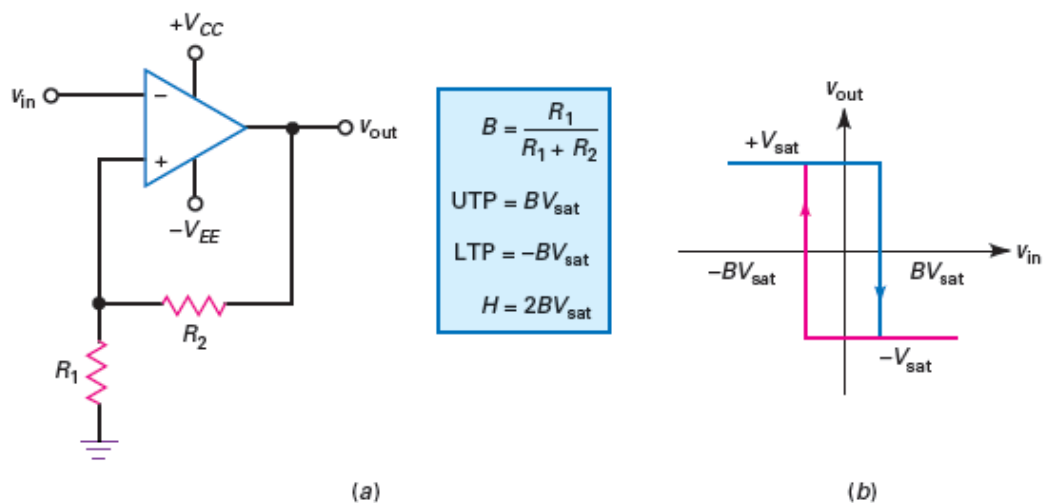


Figure 1: (a) Inverting Schmitt trigger; (b) input/output response has hysteresis.

The input voltage is applied to the inverting input. Because the feedback voltage at the non-inverting input is aiding the input voltage, the feedback is *positive*. A comparator using positive feedback like this is usually called a **Schmitt trigger**.

When the comparator is positively saturated, a positive voltage is fed back to the non-inverting input. This positive feedback voltage holds the output in the high state. Similarly, when the output voltage is negatively saturated, a negative voltage is fed back to the non-inverting input, holding the output in the low state. In either case, the positive feedback reinforces the existing output state. The feedback fraction is:

$$\beta = \frac{R1}{R1 + R2}$$

When the output is positively saturated, the reference voltage applied to the non-inverting input is $V_{\text{ref}} = +\beta V_{\text{sat}}$. When the output is negatively saturated, the reference voltage is $V_{\text{ref}} = -\beta V_{\text{sat}}$

The output voltage will remain in a given state until the input voltage exceeds the reference voltage for that state. For instance, if the output is positively saturated, the reference voltage is $+\beta V_{\text{sat}}$. The input voltage must be increased to slightly more than $+\beta V_{\text{sat}}$ to switch the output voltage from positive to negative, as shown in Fig. 1 (b). Once the output is in the negative state, it will remain there indefinitely until the input voltage becomes more negative than $-\beta V_{\text{sat}}$. Then, the output switches from negative to positive (Fig. 1b).

Hysteresis

The unusual response of Fig.1 (b) has a useful property called **hysteresis**. In Fig.1(b), the trip points are defined as the two input voltages where the output voltage changes states. The *upper trip point (UTP)* has the value

$$\text{UTP} = +\beta V_{\text{sat}}$$

and the *lower trip point (LTP)* has the value

$$\text{LTP} = -\beta V_{\text{sat}}$$

The difference between these trip points is defined as the hysteresis (also called the *dead band*):

$$\begin{aligned} H &= \text{UTP} - \text{LTP} \\ H &= +\beta V_{\text{sat}} - (-\beta V_{\text{sat}}) \\ H &= 2 \beta V_{\text{sat}} \end{aligned}$$